Εθνικό Μετσόβιο Πολυτεχνείο, ΣΗΜΜΥ Ψηφιακά Συστήματα VLSI

6η Εργαστηριακή Άσκηση "Υλοποίηση Debayering Φίλτρου με ΑΧΙ διεπαφή σε Zynq SoC FPGA"


Ομάδα 19

Παναγιώτης Μπέλσης, ΑΜ: 03120874 Θεοδώρα Εξάρχου, ΑΜ: 03120865

Μέρος Α

Ζητούμενο Εργαστηριακής Άσκησης

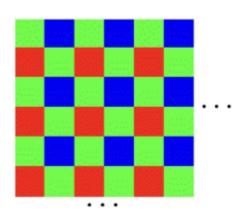Στα πλαίσια της παρούσας Εργαστηριακής Άσκησης, καλείστε να υλοποιήσετε το φίλτρο Debayering, το οποίο θα μετατρέπει την Bayer εικόνα σε RGB υπολογίζοντας τους μέσους όρους των γειτονικών pixels σε 3x3 γειτονιές. Θεωρούμε ότι το μωσαικό Bayer ακολουθεί το πρότυπο GBRG, δηλαδή η Bayer εικόνα ακολουθεί το μοτίβο που παρουσιάζεται στο Σχήμα 2.




Χωρίζουμε το κώδικα μας στα εξής μέρη

- -Debayering Filter
- -Serial to Parallel
- -Debayering box

Debayering Filter \rightarrow To Debayering φίλτρο λαμβάνει ένα pixel ανα κύκλο ρολογιου (1p/CC) με raster scan ordering και ότι η επεξεργασία (υπολογισμός μέσων όρων) πραγματοποιείται σε 3x3 γειτονιές

- <u>clk</u>: το σήμα ρολογιού, με βάση το οποίο συγχρονίζεται όλο το κύκλωμα.
- •<u>rst_n</u>: το ασύγχρονο σήμα μηδενισμού, με βάση το οποίο μηδενίζονται οι καταχωρητές και οι έξοδοι του κυκλώματος. Ενεργοποιείται στο λογικό '0'. Κατά τη λειτουργία του κυκλώματος, είναι απενεργοποιημένο (βρίσκεται μόνιμα στο λογικό '1').
- <u>pixel[7:0]</u>: σήμα εισόδου των 8 bits, το οποίο τροφοδοτεί το κύκλωμα με τα 8-bit pixels της Bayer εικόνας.
- <u>valid_in:</u> σήμα εισόδου, το οποίο ενεργοποιείται (στο λογικό '1') για να υποδείξει ότι η τιμή του σήματος pixel είναι έγκυρη. Ενεργοποιείται για αριθμό κύκλων ρολογιού ίσο με το μέγεθος της εικόνας.
- <u>new image</u>: σήμα εισόδου, το οποίο ενεργοποιείται (στο λογικό '1') για 1 κύκλο ρολογιού ταυτόχρονα με το πρώτο valid_in σήμα, ώστε να υποδείξει ότι θα αρχίσει η επεξεργασίας μιας νέας εικόνας.
- <u>R[7:0]</u>. <u>G[7:0]</u>. <u>B[7:0]</u>: σήματα εξόδου των 8 bits, τα οποία υποδεικνύουν τις χρωματικές συνιστώσες. Για κάθε pixel, εμφανίζονται ταυτόχρονα στην έξοδο και οι τρεις χρωματικές συνιστώσες. Επίσης, με βάση την λειτουργία του Debayering φιλτρου, για κάθε pixel, κάποιο από τα R, G, και B θα έχει την τιμή του σήματος pixel, ενώ τα άλλα δύο θα υπολογίζονται με τους μέσους όρους των γειτονικών pixels.
- <u>valid_out</u>: σήμα εξόδου, το οποίο ενεργοποιείται (στο λογικό '1') για να υποδείξει ότι οι τιμές των σημάτων R, G, B είναι έγκυρες. Ενεργοποιείται για αριθμό κύκλων ρολογιού ίσο με το μέγεθος της εικόνας.
- <u>image finished</u>: σήμα εξόδου, το οποίο ενεργοποιείται (στο λογικό '1') για 1 κύκλο ρολογιού ταυτόχρονα με το τελευταίο valid_out σήμα, ώστε να υποδείξει ότι η επεξεργασία της εικόνας τελείωσε.

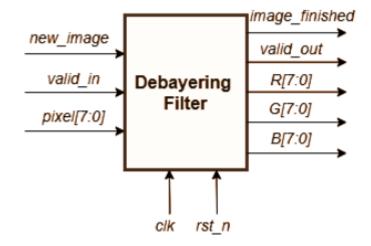


Ιεράρχηση των αρχείων μας για το design:

```
∨ □ Design Sources (1)

    ✓ ■ Debayering_Filter(Behavioral) (wrapper.vhd) (2)

✓ ■ S2P: ramruns(Behavioral) (s2p.vhd) (14)
              dffdelay1 : dff(Behavioral) (dff.vhd)
              dffdelay2 : dff(Behavioral) (dff.vhd)
            > 7 RAM_FIFO_0: fifo_generator_0 (fifo_generator_0.xci)
            > \Pi = RAM_FIFO_1: fifo_generator_0 (fifo_generator_0.xci)
            > 🕆 🔳 RAM_FIFO_2 : fifo_generator_0 (fifo_generator_0.xci)
              dff00 : dff(Behavioral) (dff.vhd)
              dff01: dff(Behavioral) (dff.vhd)
              dff02 : dff(Behavioral) (dff.vhd)
              dff10 : dff(Behavioral) (dff.vhd)
              dff11: dff(Behavioral) (dff.vhd)
              dff12 : dff(Behavioral) (dff.vhd)
              dff20 : dff(Behavioral) (dff.vhd)
              dff21 : dff(Behavioral) (dff.vhd)
              dff22 : dff(Behavioral) (dff.vhd)
          debayer_box : debayer(Behavioral) (debayer.vhd)
> Constraints
```

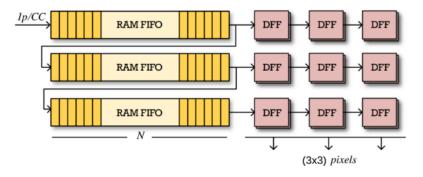Serial to Parallel \rightarrow Μετατροπέας σειριακού-σε-παράλληλο (serial-to-parallel converter). Το κύκλωμα του μετατροπέα περιλαμβάνει προσωρινή μνήμη (buffers) και μία συστοιχία από καταχωρητές (registers), ώστε να αποθηκεύει τα pixels εισόδου και να τροφοδοτεί την είσοδο του κυκλώματος υπολογισμού των μέσων όρων με όλα τα pixels της 3x3 γειτονιάς παράλληλα.



RamRuns (Serial-to-parallel)

Η "ramruns" σχεδιάζει ένα block που φροντίζει για την παραλληλοποίηση των σειριακών pixels με την χρήση 3 ram fifo και 9 βασικών DFF με βάση την σχεδίαση που προτάθηκε στην εκφώνηση. Επιπλέον χρησιμοποιήθηκαν άλλα 2 DFF για να καθυστερήσουμε την είσοδο των δεδομένων στην πρώτη Ram, έτσι ώστε να πετύχουμε καλύτερο συγχρονισμό των Ram με το ολικό κύκλωμα.

Τρέχοντας στο χαρτί το πώς γεμίζουν οι Rams και βλέποντας το πότε βγάζουν τα πρώτα δεδομένα, είδαμε ότι το πρώτο αποτέλεσμα βγαίνει στον 2N+2 κύκλο, και έπειτα σε κάθε κύκλο ρολογιού είχαμε νέο αποτέλεσμα.

Αρχικά όλα τα σήματα write, read enable είναι αρχικοποιημένα στο 0.

Atto $1 \rightarrow N cc$

```
óταν valid_in=1
write_enable0=1
read enable0=0
```

Aπό N +1 \rightarrow 2N cc

```
write_enable0=1 read_enable0=1 write_enable1=1
```

A π ó 2N+1 \rightarrow 3N cc

```
write_enable0=1
read_enable0=1
write_enable1=1
read_enable1=1
write_enable2=1
```

Στον 2N+2 cc

έχουμε το πρώτο valid_out=1 αποτέλεσμα.

A π ó 3N+1 \rightarrow 2N+1 + N*N cc

```
write_enable0=1
read_enable0=1
write_enable1=1
read_enable1=1
write_enable2=1
read_enable2=1
```

Οι παραπάνω θεωρητικές τιμές δεν αντικατοπτρίζουν στο 100% την συμπεριφορά των ram στο simulation καθώς στό χαρτί θεωρούμε ότι τα σήματα write, read enable αποκτούν αμέσως την τιμή που τους δίνουμε, κάτι που στην πραγματικότητα έχει καθυστέρηση ενός κύκλου.

Αφότου τρέξαμε ένα πρόγραμμα μόνο με τις rams για να καταλάβουμε το πώς γεμίζουν και το πώς διαχειρίζονται τα σήματα που τους δίνουμε καταλήξαμε στην παρακάτω υλοποίηση του κώδικα που τρέχει λίγο διαφορετικά σε σχέση με την θεωρητική υλοποίηση.

```
else if( valid_in = '1' ) then
          wr_en0 <= '1';
          counter_begin <= counter_begin + 1;</pre>
           if (to_integer(unsigned(counter_begin)) >= N-2) then
                   rd_en0 <= '1';
                   wr_en1 <='1';
           end if;
           if(to_integer(unsigned(counter_begin)) >= 2*N-3) then
                   rd_en1 <='1';
           end if;
           if(to_integer(unsigned(counter_begin)) >= 2*N-2) then
                   wr_en2 <='1';
           end if;
           if(to_integer(unsigned(counter_begin)) >= 3*N-3) then
                      rd_en2 <='1';
           end if;
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
use IEEE.NUMERIC STD.ALL;
use ieee.math real.all;
entity ramruns is
    generic ( N: integer := 32 );
    port (
        clk : IN STD_LOGIC;
        rst : IN STD_LOGIC;
        pixel : IN STD LOGIC VECTOR(7 DOWNTO 0);
        col,row : OUT std logic vector(integer(ceil(log2(real(N))))-1
downto 0) := (others => '0');
        s00 : OUT STD LOGIC VECTOR(7 DOWNTO 0);
        s01 : OUT STD LOGIC VECTOR(7 DOWNTO 0) ;
        s02 : OUT STD_LOGIC_VECTOR(7 DOWNTO 0) ;
        s10 : OUT STD_LOGIC_VECTOR(7 DOWNTO 0) ;
        s11 : OUT STD_LOGIC_VECTOR(7 DOWNTO 0);
        s12 : OUT STD_LOGIC_VECTOR(7 DOWNTO 0) ;
        s20 : OUT STD_LOGIC_VECTOR(7 DOWNTO 0) ;
        s21 : OUT STD LOGIC VECTOR(7 DOWNTO 0) ;
        s22 : OUT STD_LOGIC_VECTOR(7 DOWNTO 0);
        valid_in,new_image : IN STD_LOGIC; --signals when it is valid to
start the multiplication process
        image_finished: OUT STD_LOGIC := '0';
        valid_out: OUT STD_LOGIC;
        out row , out col : OUT
std logic vector(integer(ceil(log2(real(N))))-1 downto 0) := (others
=> '0')
    );
end ramruns;
architecture Behavioral of ramruns is
  COMPONENT fifo_generator_0
  Port (
    clk : in STD LOGIC;
    srst : in STD LOGIC;
    din : in STD_LOGIC_VECTOR ( 7 downto 0 );
```

```
wr en : in STD LOGIC;
   rd_en : in STD_LOGIC;
   dout : out STD_LOGIC_VECTOR ( 7 downto 0 );
   full : out STD LOGIC;
   empty : out STD LOGIC
 );
END COMPONENT;
component dff is
   port(
     d : in std_logic_vector(7 downto 0);
     q : out std logic vector(7 downto 0);
     clk : in std_logic;
     rst : in std_logic
     );
end component;
signal ram_out_2, ram_out_1, ram_out_0 : std_logic_vector(7 downto 0) :=
(others => '0');
signal rd en0: std logic := '0';
signal rd en1: std logic := '0';
signal rd_en2: std_logic := '0';
signal wr_en0: std_logic := '0';
signal wr_en1: std_logic := '0';
signal wr en2: std logic := '0';
signal t1,t2,t3,t4,t5,t6,t7,t8,t9 : STD_LOGIC_VECTOR(7 DOWNTO 0) :=
(others => '0');
signal full0, full1, full2, empty0, empty1, empty2: std_logic;
signal pixel_delay1 ,pixel_delay2 : STD_LOGIC_VECTOR(7 DOWNTO 0) :=
(others => '0');
signal col temp,row temp :
std_logic_vector(integer(ceil(log2(real(N))))-1 downto 0) := (others =>
'0');
signal col_signal : std_logic_vector(integer(ceil(log2(real(N)))))-1
downto 0) := (others => '0');
signal counter_begin : std_logic_vector(integer(ceil(log2(real(N*N))))
downto 0) := (others => '0');
begin
dffdelay1 : dff port map(d=>pixel, clk=>clk, rst=>rst, q=>pixel_delay1
);
```

```
dffdelay2 : dff port map(d=>pixel delay1, clk=>clk, rst=>rst,
q=>pixel_delay2 );
RAM_FIFO_0 : fifo_generator_0
    PORT MAP (
        clk \Rightarrow clk,
        srst => rst,
        din => pixel_delay2,
        wr_en => wr_en0,
        rd_en => rd_en0,
        dout => ram out 0,
        full => full0,
        empty => empty0
    );
RAM_FIFO_1 : fifo_generator_0
PORT MAP (
   clk \Rightarrow clk,
    srst => rst,
    din => ram_out_0,
    wr en => wr en1,
    rd_en => rd_en1,
    dout => ram_out_1,
    full => full1,
    empty => empty1
);
RAM FIFO 2 : fifo generator 0
PORT MAP (
    clk \Rightarrow clk,
    srst => rst,
    din => ram_out_1,
    wr_en => wr_en2,
    rd_en => rd_en2,
    dout => ram_out_2,
    full => full2,
    empty => empty2
);
dff00 : dff port map(d=>ram out 0, clk=>clk, rst=>rst, q=>t1);
 s00 <=t1;
dff01 : dff port map(d=>t1, clk=>clk, rst=>rst, q=>t2);
s01 <=t2;
dff02 : dff port map(d=>t2, clk=>clk, rst=>rst, q=>t3);
 s02 <=t3;
```

```
dff10 : dff port map(d=>ram out 1, clk=>clk, rst=>rst, q=>t4);
s10 <=t4;
dff11 : dff port map(d=>t4, clk=>clk, rst=>rst, q=>t5);
s11 <=t5;
dff12 : dff port map(d=>t5, clk=>clk, rst=>rst, q=>t6);
s12 <=t6;
dff20 : dff port map(d=>ram_out_2, clk=>clk, rst=>rst, q=>t7);
s20 <=t7;
dff21 : dff port map(d=>t7,clk=>clk, rst=>rst, q=>t8);
s21 <=t8;
dff22 : dff port map(d=>t8, clk=>clk, rst=>rst, q=>t9);
s22 <=t9;
 process(clk,rst)
 --constant N : integer :=32;
 begin
   if( rst = '1') then
                  wr_en0 <= '0';
                  rd_en0 <= '0';
                  wr_en1 <= '0';
                  rd_en1 <= '0';
                  wr en2 <= '0';
                  rd_en2 <= '0';
                  counter_begin <=(others => '0');
                  row<= (others => '0');
                  col <= (others => '0');
     --RESET
    elsif rising_edge(clk) then
           valid_out <='0';</pre>
           image_finished <='0';</pre>
       if (valid_in = '1' AND new_image ='1' ) then
           counter_begin <= (others => '0');
           row_temp<= (others => '0');
           col_temp <= (others => '0');
           image_finished <='0';</pre>
```

```
else if( valid_in = '1' ) then
          wr_en0 <= '1';
           counter begin <= counter begin + 1;</pre>
            if (to_integer(unsigned(counter_begin)) >= N-2) then
                    rd en0 <= '1';
                    wr en1 <='1';
            end if;
            if(to_integer(unsigned(counter_begin)) >= 2*N-3) then
                    rd_en1 <='1';
            end if;
            if(to_integer(unsigned(counter_begin)) >= 2*N-2) then
                    wr_en2 <='1';
            end if;
            if(to_integer(unsigned(counter_begin)) >= 3*N-3) then
                       rd_en2 <='1';
            end if;
    if( counter_begin > 2*N +1) then
              valid_out <='1';</pre>
              col_signal <=col_temp;</pre>
              if(row_temp = 0 and col_temp = 0) then
                 col <= col_temp + 1;</pre>
              else
                 col <= col temp+1;</pre>
              end if;
              row <= row temp;</pre>
              out_row <= row_temp;</pre>
              out_col <= col_temp;</pre>
              col_temp <= col_temp+1;</pre>
              if (to_integer(unsigned(col_signal)) = N-2) then --allazw
grammh
                    row_temp <= row_temp + 1;</pre>
                    col temp <= (others => '0');
              end if;
              if (to_integer(unsigned(row_temp)) = N-1 and
to_integer(unsigned(col_temp)) = N-1) then
                     image_finished <= '1';</pre>
              end if;
```

```
end if;
end if;
end if;
end if;
end process;
end Behavioral;
```

DFF

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.std_logic_unsigned.all;
--DFF for 8 bit pixel
entity dff is
    Port ( d : in STD_LOGIC_VECTOR (7 downto 0);
           clk : in STD_LOGIC;
           rst : in STD_LOGIC;
           q : out STD_LOGIC_VECTOR (7 downto 0));
end dff;
architecture Behavioral of dff is
begin
    process(clk, rst) begin
        if rst='1' then
            Q<="00000000";
        elsif rising_edge(clk) then
            Q <= D;
        end if;
    end process;
end Behavioral;
```

Debayering box \rightarrow Δέχεται το 3x3 παράθυρο, πρώτα ελέγχεται αν κάποιο pixel πρέπει να θεωρηθεί 0 βάσει της θέσης που έχει το pixel που επεξεργαζόμαστε τη δεδομένη στιγμή, αντιστρέφουμε το πίνακα που δημιουργήσαμε στο ramruns(Serial to Parallel) έτσι ώστε να έχει τη σωστή μορφή.





architecture Behavioral of debayer is





Ύστερα υπολογίζει τους 4 δυνατούς μέσους (γραμμή, στήλη, σταυρός, γωνιακά) και τέλος βάσει του state τα RGB παίρνουν τιμές είτε από τους παραπάνω υπολογισμούς είτε απευθείας από το μεσαίο pixel του παραθύρου.

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD LOGIC UNSIGNED.ALL;
use IEEE.NUMERIC_STD.ALL;
use ieee.math_real.all;
entity debayer is
  generic( N: integer := 32);
 Port (
 clk : IN STD LOGIC;
 rst: IN STD LOGIC;
 s2p_00 : IN STD_LOGIC_VECTOR(7 DOWNTO 0);
  s2p_01 : IN STD_LOGIC_VECTOR(7 DOWNTO 0);
 s2p 02 : IN STD LOGIC VECTOR(7 DOWNTO 0);
 s2p_10 : IN STD_LOGIC_VECTOR(7 DOWNTO 0);
 s2p_11 : IN STD_LOGIC_VECTOR(7 DOWNTO 0);
 s2p 12 : IN STD LOGIC VECTOR(7 DOWNTO 0);
  s2p_20 : IN STD_LOGIC_VECTOR(7 DOWNTO 0);
 s2p_21 : IN STD_LOGIC_VECTOR(7 DOWNTO 0);
 s2p_22 : IN STD_LOGIC_VECTOR(7 DOWNTO 0);
 line_img : IN std_logic_vector(integer(ceil(log2(real(N)))))-1 downto
0);
 column_img : IN std_logic_vector(integer(ceil(log2(real(N))))-1 downto
0);
 R : out std_logic_vector(7 downto 0);
 G : out std_logic_vector(7 downto 0);
 B : out std_logic_vector(7 downto 0)
  );
end debayer;
```

```
signal box 00, box 01, box 02, box 10, box 11, box 12, box 20, box 21,
box_22 : std_logic_vector(7 downto 0);
signal add_outer, add_cross,add_row,add_col : std_logic_vector(7 downto
0);
signal add_row_bef, add_col_bef: std_logic_vector(8 downto 0);
signal add_outer_bef, add_cross_bef: std_logic_vector(9 downto 0);
signal unsigned_x1,unsigned_x2,unsigned_x3,unsigned_x4 : unsigned(7
downto 0);
signal sum_unsigned : unsigned(8 downto 0);
signal divided_unsigned : unsigned(8 downto 0);
signal sum_unsigned_2 : unsigned(9 downto 0);
--constant N : integer := 32;
begin
box_00 <= s2p_22 when to_integer(unsigned(line_img)) /= 0 and
to_integer(unsigned(column_img)) /= 0 else (others => '0');
box_01 <= s2p_21 when to_integer(unsigned(line_img)) /= 0 else (others</pre>
=> '0');
box_02 <= s2p_20 when to_integer(unsigned(line_img)) /= 0 and</pre>
to_integer(unsigned(column_img)) /= N-1 else (others => '0'); -
box_10 <= s2p_12 when to_integer(unsigned(column_img)) /= 0 else (others</pre>
=> '0');
box_11 <= s2p_11;
box_12 <= s2p_10 when to_integer(unsigned(column_img)) /= N-1 else</pre>
(others => '0');
box 20 <= s2p 02 when to integer(unsigned(line img)) /= N-1 and
to_integer(unsigned(column_img)) /= 0 else (others => '0');
box_21 <= s2p_01 when to_integer(unsigned(line_img)) /= N-1 else</pre>
(others => '0');
box_22 <= s2p_00 when to_integer(unsigned(line_img)) /= N-1 and</pre>
to_integer(unsigned(column_img)) /= N-1 else (others => '0');
add_row_bef <= ('0' & box_10) + ('0' & box_12); --kanw to add_row_bef 9
bits
add_row <= add_row_bef(8 downto 1); -- me leftshift kanw /2</pre>
add_col_bef <= ('0' & box_01) + ('0' & box_21);
add_col <= add_col_bef(8 downto 1);</pre>
add_cross_bef <= ("00" & box_01) + ("00" & box_10) + ("00" & box_12) +
("00" & box 21);
add_cross <= add_cross_bef(9 downto 2); -- 2 leftshift ara kanw /4
add_outer_bef <= ("00" & box_00) + ("00" & box_02) + ("00" & box_20) +
```

```
("00" & box 22);
add_outer <= add_outer_bef(9 downto 2);</pre>
 process(clk,rst)
    begin
         if rising_edge(clk) then
             if line_img(0) = '0' and column_img(0) = '0' then -- (ii)
                      R <= add_col;</pre>
                      G <= box_11;
                      B <= add_row;</pre>
             elsif line_img(0) = '0' and column_img(0) = '1' then --(iv)
                      R <= add_outer;</pre>
                      G <= add_cross;</pre>
                      B <= box_11;
            elsif line_img(\emptyset) = '1' and column_img(\emptyset) = '0' then --(iii)
                     R <= box_11;
                     G <= add cross;
                     B <= add_outer;</pre>
            elsif line_img(0) = '1' and column_img(0) = '1' then --(i)
                    R <= add_row;</pre>
                    G \leftarrow box 11;
                    B <= add_col;</pre>
            end if;
            end if;
      end process;
end Behavioral;
```

Ο κώδικας του "Debayering_Filter" αρχείου είναι το συνολικό wrapper που κάνει το mapping των κοινών σημάτων του "ramruns" με του "debayer".

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD LOGIC UNSIGNED.ALL;
use IEEE.NUMERIC_STD.ALL;
use ieee.math_real.all;
entity Debayering_Filter is
  generic( N: integer :=32 );
  Port (
  clk : IN STD LOGIC;
  rst : IN STD_LOGIC;
  pixel : IN STD_LOGIC_VECTOR(7 DOWNTO 0);
  valid in, new image: IN STD LOGIC; -- signals when it is valid to start
the multiplication process
  R : OUT STD_LOGIC_VECTOR(7 DOWNTO 0);
 G : OUT STD LOGIC VECTOR(7 DOWNTO 0);
  B : OUT STD LOGIC VECTOR(7 DOWNTO 0);
  --outputs :out STD_LOGIC_VECTOR(31 DOWNTO 0):= (others => '0');
 valid_out: OUT STD_LOGIC;
  image_finished: OUT STD_LOGIC;
  out row all , out col all : OUT
std_logic_vector(integer(ceil(log2(real(N))))-1 downto 0) := (others
=> '0')
  ); -----fdsfs
end Debayering_Filter;
architecture Behavioral of Debayering Filter is
component ramruns is
    generic ( N: integer := 32 );
    port (
        clk : IN STD_LOGIC;
        rst : IN STD_LOGIC;
        pixel : IN STD_LOGIC_VECTOR(7 DOWNTO 0);
        valid_in,new_image : IN STD_LOGIC; --signals when it is valid to
start the multiplication process
        s00 : OUT STD LOGIC VECTOR(7 DOWNTO 0);
        s01 : OUT STD LOGIC VECTOR(7 DOWNTO 0);
        s02 : OUT STD_LOGIC_VECTOR(7 DOWNTO 0);
        s10 : OUT STD LOGIC VECTOR(7 DOWNTO 0);
```

```
s11 : OUT STD LOGIC VECTOR(7 DOWNTO 0);
        s12 : OUT STD_LOGIC_VECTOR(7 DOWNTO 0);
        s20 : OUT STD_LOGIC_VECTOR(7 DOWNTO 0);
        s21 : OUT STD LOGIC VECTOR(7 DOWNTO 0);
        s22 : OUT STD LOGIC VECTOR(7 DOWNTO 0);
        col,row : OUT std_logic_vector(integer(ceil(log2(real(N))))-1
downto 0) := (others => '0');
       valid out: OUT STD LOGIC;
        image_finished: OUT STD_LOGIC;
        out_row , out_col : OUT
std_logic_vector(integer(ceil(log2(real(N))))-1 downto 0) := (others
=> '0')
    );
end component;
component debayer is
  generic ( N: integer := 32 );
 Port (
 clk : IN STD_LOGIC;
 rst: IN STD LOGIC;
 s2p 00 : IN STD LOGIC VECTOR(7 DOWNTO 0);
 s2p_01 : IN STD_LOGIC_VECTOR(7 DOWNTO 0);
 s2p_02 : IN STD_LOGIC_VECTOR(7 DOWNTO 0);
 s2p_10 : IN STD_LOGIC_VECTOR(7 DOWNTO 0);
 s2p 11 : IN STD LOGIC VECTOR(7 DOWNTO 0);
 s2p_12 : IN STD_LOGIC_VECTOR(7 DOWNTO 0);
 s2p_20 : IN STD_LOGIC_VECTOR(7 DOWNTO 0);
 s2p 21 : IN STD LOGIC VECTOR(7 DOWNTO 0);
 s2p 22 : IN STD LOGIC VECTOR(7 DOWNTO 0);
 line_img : IN std_logic_vector(integer(ceil(log2(real(N)))))-1 downto
0);
 column img : IN std logic vector(integer(ceil(log2(real(N)))))-1 downto
0);
 R : out std_logic_vector(7 downto 0);
 G : out std_logic_vector(7 downto 0);
 B : out std_logic_vector(7 downto 0)
  );
end component;
--constant N : integer := 32;
signal clk_signal, rst_signal: STD_LOGIC;
signal s00_signal, s01_signal, s02_signal, s10_signal, s11_signal,
s12 signal: std logic vector(7 downto 0) := (others => '0');
signal s20_signal, s21_signal, s22_signal: std_logic_vector(7 downto 0)
:= (others => '0');
```

```
signal col signal, row signal:
std_logic_vector(integer(ceil(log2(real(N))))-1 downto 0);
signal out_col_signal, out_row_signal:
std logic vector(integer(ceil(log2(real(N))))-1 downto 0);
--signal Rsig : STD_LOGIC_VECTOR(7 DOWNTO 0) := (others => '0');
--signal Gsig : STD_LOGIC_VECTOR(7 DOWNTO 0) := (others => '0');
--signal Bsig : STD_LOGIC_VECTOR(7 DOWNTO 0) := (others => '0');
begin
S2P : ramruns
    generic map (N \Rightarrow N)
    port map(
    clk => clk,
    rst => rst,
    pixel => pixel,
    valid_in => valid_in,
    new image => new image,
    s00 => s00_signal,
    s01 => s01_signal,
    s02 => s02 signal,
    s10 => s10 signal,
    s11 => s11_signal,
    s12 => s12_signal,
    s20 => s20_signal,
    s21 => s21 signal,
    s22 => s22_signal,
    valid_out => valid_out,
   image finished => image finished,
    row => row signal,
    col => col_signal,
    out_row => out_row_all,
    out_col => out_col_all
    );
debayer box : debayer
    generic map ( N => N )
    port map(
        clk \Rightarrow clk,
        rst => rst,
        s2p_00 => s00_signal,
        s2p 01 \Rightarrow s01 signal,
        s2p_02 \Rightarrow s02_signal,
        s2p_10 => s10_signal,
```

```
s2p_11 => s11_signal,
s2p_12 => s12_signal,
s2p_20 => s20_signal,
s2p_21 => s21_signal,
s2p_22 => s22_signal,
line_img => row_signal,
column_img => col_signal,
R => R,
G => G,
B => B);
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD LOGIC UNSIGNED.ALL;
use IEEE.NUMERIC_STD.ALL;
use ieee.math real.all;
use STD.TEXTIO.ALL;
entity Debayering_Filter_tb is
end Debayering_Filter_tb;
architecture test_bench of Debayering_Filter_tb is
 constant N_tb : integer := 32;
 component Debayering_Filter
 Port (
 clk : IN STD LOGIC;
 rst : IN STD LOGIC;
 pixel : IN STD_LOGIC_VECTOR(7 DOWNTO 0);
  valid_in,new_image : IN STD_LOGIC; --signals when it is valid to start
the multiplication process
  R : OUT STD_LOGIC_VECTOR(7 DOWNTO 0);
 G : OUT STD_LOGIC_VECTOR(7 DOWNTO 0);
 B : OUT STD_LOGIC_VECTOR(7 DOWNTO 0);
  --outputs :out STD_LOGIC_VECTOR(31 DOWNTO 0):= (others => '0');
 valid out: OUT STD LOGIC;
  image_finished: OUT STD_LOGIC;
                                          out col all
                                                                      OUT
               out row all
std_logic_vector(integer(ceil(log2(real( N_tb))))-1 downto 0)
                                                                      :=
(others => '0')
  );
end component;
 -- Input Signals
 signal clk : std_logic := '0';
 signal rst: std_logic := '0';
 signal valid in : std logic := '1';
 signal new_image: std_logic := '0';
 signal pixel : STD_LOGIC_VECTOR(7 DOWNTO 0);
 -- Output Signals
 signal R : STD_LOGIC_VECTOR(7 DOWNTO 0);
 signal G : STD LOGIC VECTOR(7 DOWNTO 0);
 signal B : STD_LOGIC_VECTOR(7 DOWNTO 0);
 signal image_finished: STD_LOGIC;
 signal valid out : std logic := '0';
```

```
signal
                               out col signal,
                                                            out row signal:
std_logic_vector(integer(ceil(log2(real(N_tb))))-1 downto 0);
 -- CLock
 constant CLK PERIOD : time := 10ns;
 -- File I/O
     file
           input_file
                                      text open
                                                          read_mode
                                                                       is
"C:\Users\basok\Desktop\input.txt";
               output file
                                                          write_mode
                                      text
                                                open
                                                                          is
"C:\Users\basok\Desktop\output.txt";
wrapper_instance: Debayering_Filter
 port map(
 clk => clk,
 rst => rst,
 pixel => pixel,
 valid in => valid in,
 new_image => new_image,
 R \Rightarrow R,
 B \Rightarrow B,
 G \Rightarrow G
 image_finished => image_finished,
 valid_out => valid_out,
  out_row_all =>out_row_signal ,
  out col all =>out col signal
 );
 clk_proc: process
 begin
 clk <= '0';
 wait for CLK_PERIOD / 2;
 clk <= '1';
 wait for CLK_PERIOD / 2;
 end process;
 CHANGE_RST_validin: process
 begin
 rst <= '0';
 valid_in <= '1';</pre>
 wait for N_tb * N_tb * CLK_PERIOD;
 end process;
 CHANGE_new_image: process
 begin
```


```
new image <= '1';</pre>
 wait for CLK_PERIOD;
 new_image <= '0';</pre>
 wait for ((2*N tb +3+ (N tb * N tb ))* CLK PERIOD) - CLK PERIOD;
 end process;
 -- Read pixel values from input file
 READ PIXELS: process
 variable input_line : line;
 variable input_pixel : integer;
 variable end_of_file : boolean := false;
 begin
 while not end_of_file loop
   if endfile(input_file) then
    end of file := true;
    readline(input_file, input_line);
    read(input line, input pixel);
    pixel <= std_logic_vector(to_unsigned(input_pixel, 8));</pre>
   wait for CLK_PERIOD;
  end if;
 end loop;
 wait;
 end process;
 -- Write RGB values to output file
WRITE_OUTPUTS: process
 variable output_line : line;
 begin
 while true loop
  wait until clk'event and clk = '1';
   if valid out = '1' then
    write(output_line, integer'image(to_integer(unsigned(R))));
    write(output_line, string'(" "));
    write(output_line, integer'image(to_integer(unsigned(G))));
    write(output_line, string'(" "));
    write(output_line, integer'image(to_integer(unsigned(B))));
    writeline(output_file, output_line);
  end if;
  end loop;
 end process;
end test_bench;
```

Τρέξαμε το φίλτρο με N=32, αλλά έχουμε διασφαλίσει ότι είναι μεταβλητό. Σε περίπτωση που θέλουμε να το αλλάξουμε, αρκεί να εισάγουμε τον επιθυμητό αριθμό. generic(N: integer := 32);

Στο testbench βαζουμε τα δεδομενα απο input.txt και τα αποτελεσματα output.txt Ελέγξαμε εαν δουλευει ο κωδικας μας με τα δεδομενα που δόθηκαν στο Helios TEST INPUT DATA




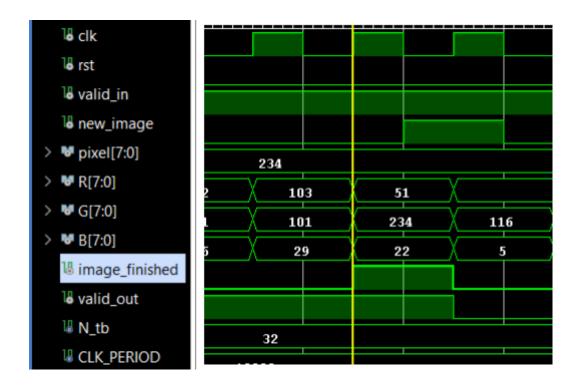Στην εικόνα παραθέτουμε το simulation για το αρχικο pixel (103) που επεξεργαζόμαστε και βλέπουμε ότι το valid_out ενεργοποιείται (στο λογικό '1') ώστε να υποδείξει ότι η επεξεργασία της εικόνας ξεκινησε.



Στην εικόνα παραθέτουμε το simulation για το τελευταίο pixel (234)που επεξεργαζόμαστε και βλέπουμε ότι το image_finished ενεργοποιείται (στο λογικό '1') για 1 κύκλο ρολογιού ταυτόχρονα με το τελευταίο valid_out σήμα, ώστε να υποδείξει ότι η επεξεργασία της εικόνας τελείωσε.

Block diagram

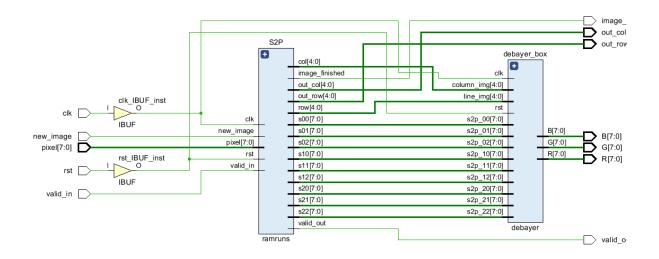

Υπολογισμός latency & throughput

Το latency Το latency είναι ο αριθμός των κύκλων που απαιτούνται από τη στιγμή που τα δεδομένα εισάγονται στο σύστημα μέχρι να εμφανιστεί μια έγκυρη έξοδος. Εχουμε


Tlatency = Tenable + Tcenter =
$$(N-2) + (N+4) + 1 \Rightarrow Tlatency = 2N + 3 clocks$$

throughput = 1 μιας και λαμβάνουμε ένα νέο και έγκυρο συνδυασμό R,G,B σε κάθε κύκλο ρολογιού έπειτα από το αρχικό latency. Ακόμη, το σύστημα είναι συνεχούς διοχέτευσης, δηλαδή μπορεί να έρθει νέα εικόνα κατά τη διάρκεια της επεξεργασίας της προηγούμενης και θα γίνεται κανονικά η έισοδος των δεδομένων της στις fifo.

Καταγραφή και ανάλυση πόρων:


• Για N=64:

Resource	Utilization	Available	Utilization %
LUT	286	17600	1.63
FF	300	35200	0.85
BRAM	1.50	60	2.50
Ю	50	100	50.00

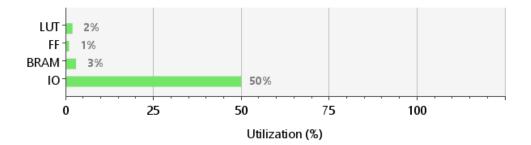

• Για N=128:

Resource	Utilization	Available	Utilization %
LUT	301	17600	1.71
FF	308	35200	0.88
BRAM	1.50	60	2.50
Ю	52	100	52.00

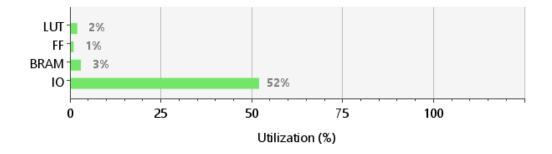

Δεν παρατηρείται κάποια διαφοροποίηση στους πόρους που χρησιμοποιούνται όταν αλλάζουμε την τιμή του Ν, καθώς τα FIFO που χρησιμοποιήθηκαν για τη μετατροπή του σειριακού σε παράλληλο έχουν μέγεθος 1024, το οποίο καλύπτει όλες τις περιπτώσεις χωρίς να προκαλείται υπερχείλιση. Επιπλέον, οι μετρητές (counters) που χρησιμοποιούνται για τον συγχρονισμό των σημάτων wr_enable και rd_enable των δύο τελευταίων FIFO παραμένουν ίδιοι, απλώς αλλάζει η μέγιστη τιμή που μπορούν να πάρουν.